 




CSL215 DIGITAL LOGIC AND SYSTEM DESIGN


Sequential Multiplier Design

Sequential shift add multiplier




```
s = 0
for i in 0 to n-1 loop
  if ( $B_0$ ) then s = s+A
end if
  A = 2 x A
  B = B / 2
end loop
```


Interface

 


Synchronizing signals

 


ASM chart for multiplier

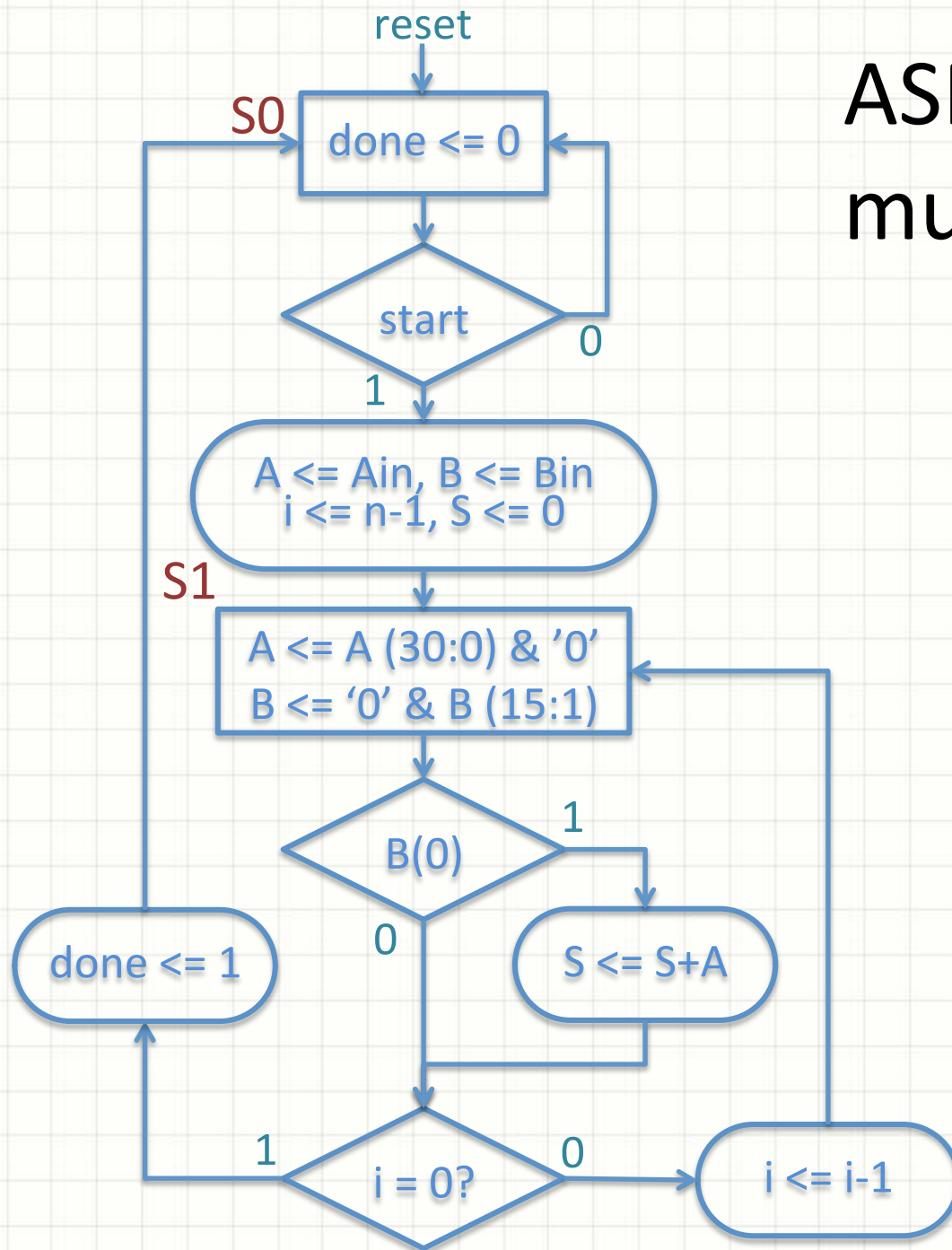


Control-data partition

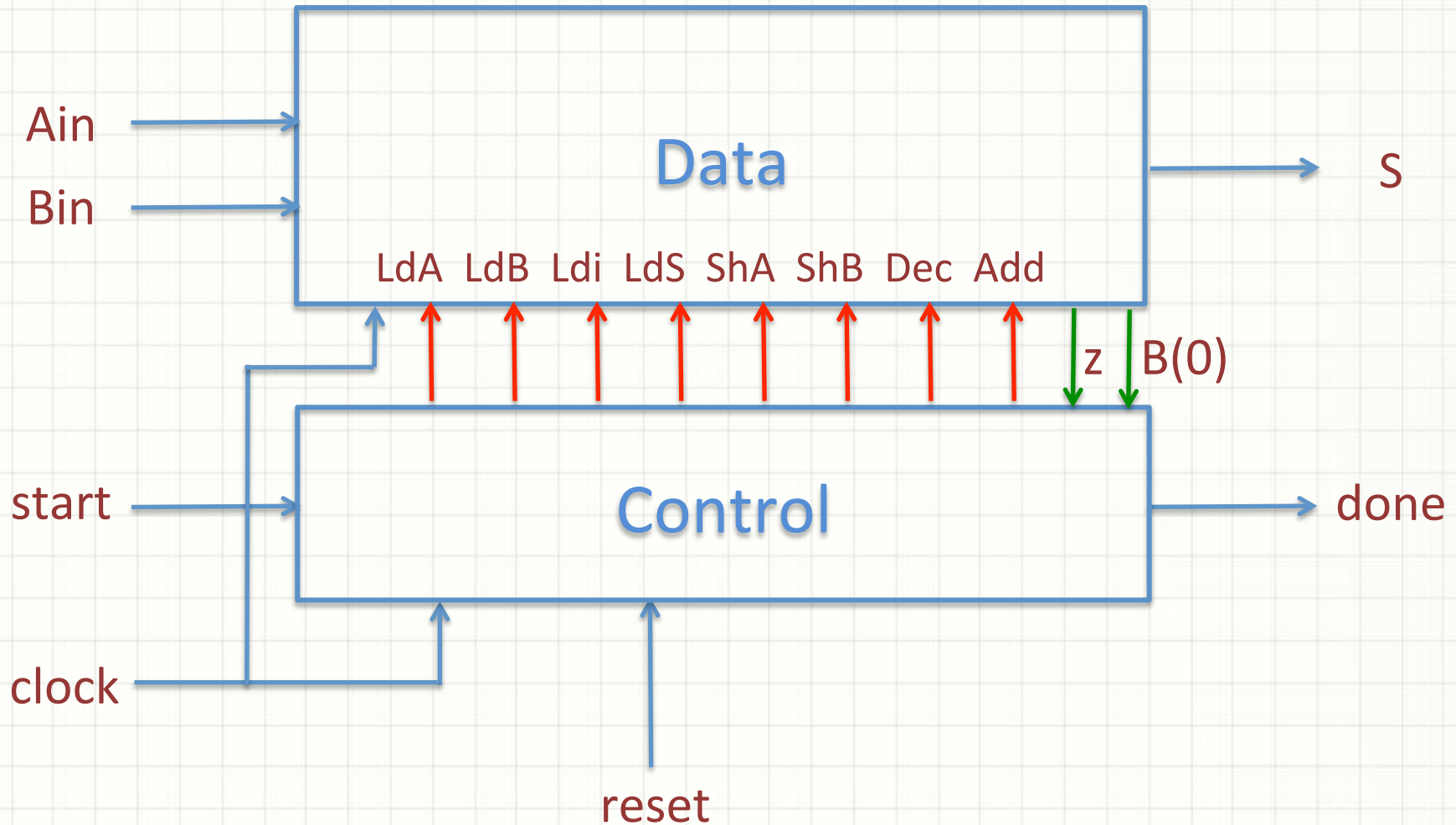

Data path

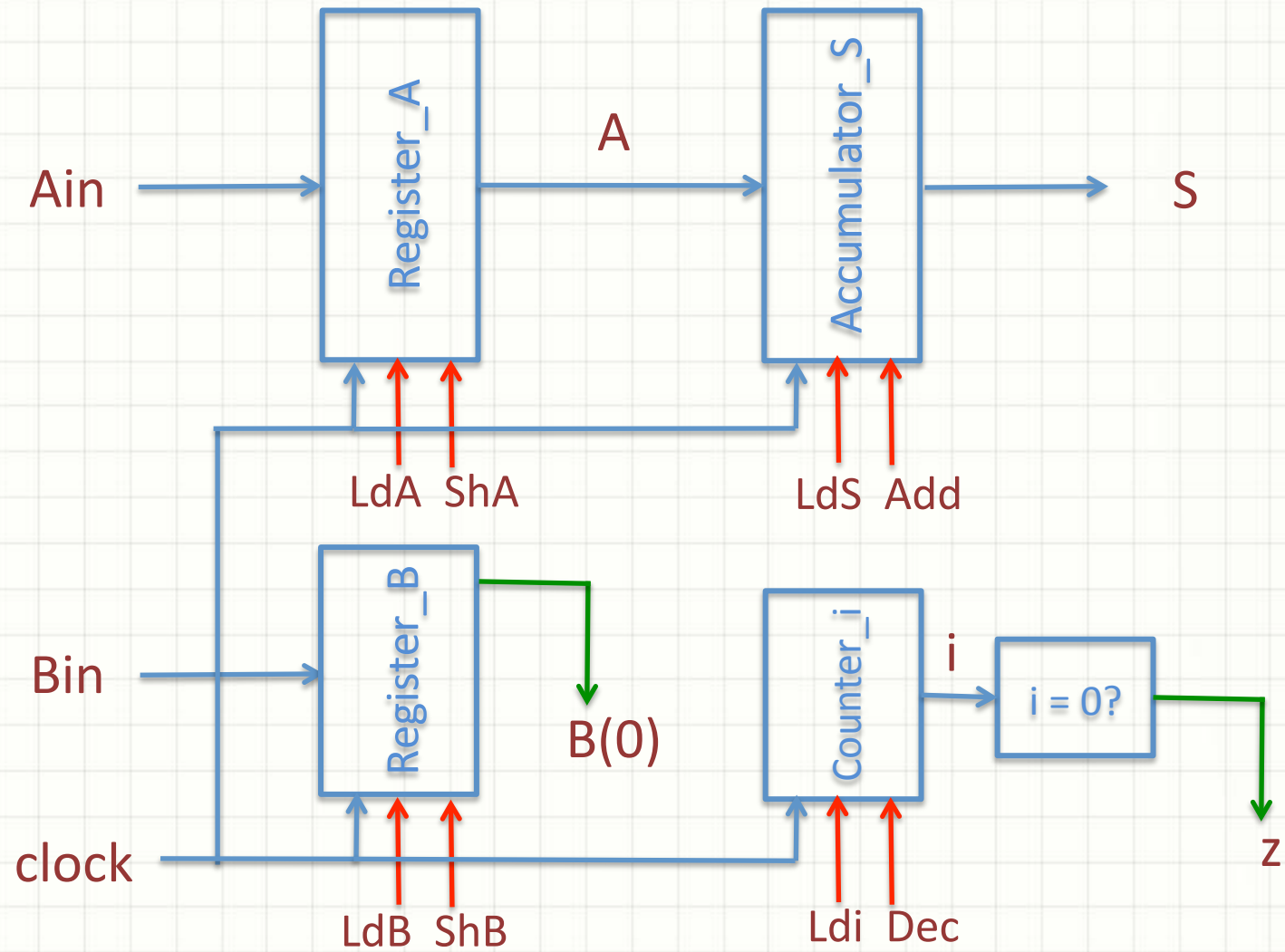

ASM chart for multiplier controller

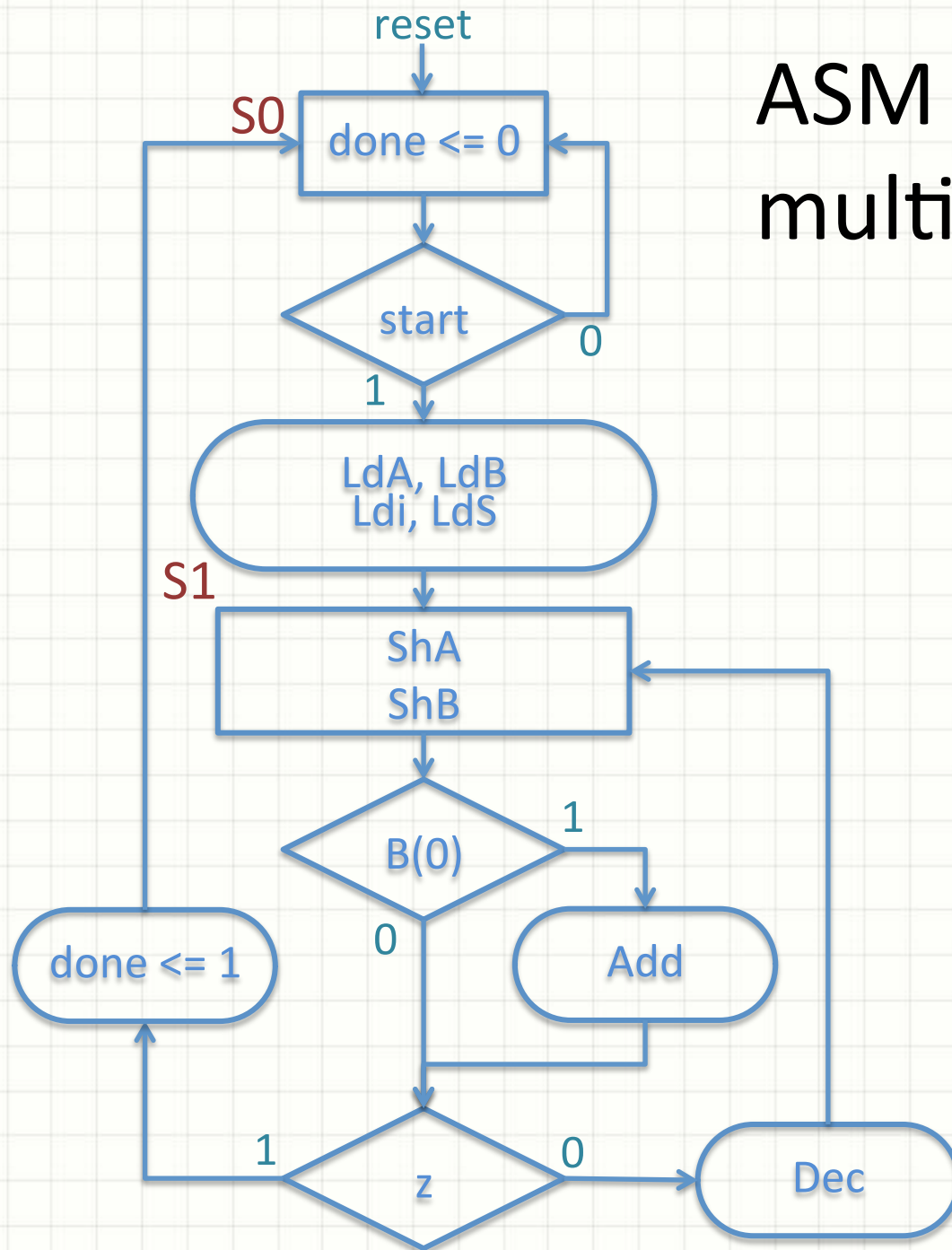

Multiplier VHDL description

```
mult_proc: process (reset, clock)
begin
    if reset = '1' then state <= S0;
    elsif (clock'event and clock = '1') then
        case state is
            when S0 =>
                . . . .
            when S1 =>
                . . . .
        end case;
    end if;
end process;
```

Multiplier VHDL description

when S0 =>

done <= '0';

if start = '1' then

A <= zero16 & Ain;

B <= Bin;

i <= n-1;

S <= zero32;

state <= S0;

end if;

Multiplier VHDL description

when S1 =>

A <= A (30 downto 0) & '0';

B <= '0' & B (15 downto 1);

if B (0) = '1' then

S <= S + A;

end if;

if i = 0 then

done <= 1;

state <= S0;

else

i <= i - 1;

end if;

Controller (state transitions) in VHDL

```
mult_control_trans_proc: process (reset, clock)
begin
    if reset = '1' then state <= S0;
    elsif (clock'event and clock = '1') then
        case state is
            when S0 =>
                if start = '1' then state <= S1; end if;
            when S1 =>
                if z = '1' then state <= S0; end if;
        end case;
    end if;
end process;
```

Controller (outputs) in VHDL

```
mult_control_out_proc: process (state, start, B, z)
```

```
begin
```

```
    LdA <= '0'; LdB <= '0'; Ldi <= '0'; LdS <= '0';
```

```
    ShA <= '0'; ShB <= '0'; Add <= '0'; Dec <= '0'; done <= '0';
```

```
    case state is
```

```
        when S0 =>
```

```
            if start = '1' then LdA <= '1'; LdB <= '1'; Ldi <= '1'; LdS <= '1';  
            end if;
```

```
        when S1 =>
```

```
            ShA <= '1'; ShB <= '1';
```

```
            if B(0) = '1' then Add <= '1'; end if;
```

```
            if z = '1' then done <= '1'; else Dec <= '1'; end if;
```

```
    end case;
```

```
end process;
```

Datapath in VHDL : Register A

```
Register_A: process (clock)
```

```
begin
```

```
    if (clock'event and clock = '1') then
```

```
        if LdA = '1' then A <= zero16 & Ain;
```

```
        elsif ShA = '1' then A <= A (30 downto 0) & '0';
```

```
        end if;
```

```
    end if;
```

```
end process;
```

Datapath in VHDL : Register B

```
Register_B: process (clock)
```

```
begin
```

```
  if (clock'event and clock = '1') then
```

```
    if LdB = '1' then B <= Bin;
```

```
    elsif ShB = '1' then B <= '0' & B (15 downto 1);
```

```
  end if;
```

```
end if;
```

```
end process;
```


Datapath in VHDL : Accumulator S

```
Accumulator_S: process (clock)
begin
    if (clock'event and clock = '1') then
        if LdS = '1' then S <= zero32;
        elsif Add = '1' then S <= S + A;
        end if;
    end if;
end process;
```

Datapath in VHDL : Counter i

```
Counter_i: process (clock)
```

```
begin
```

```
    if (clock'event and clock = '1') then
```

```
        if Ldi = '1' then i <= 0;
```

```
        elsif Dec = '1' then i <= i - 1;
```

```
        end if;
```

```
    end if;
```

```
end process;
```



THANKS